
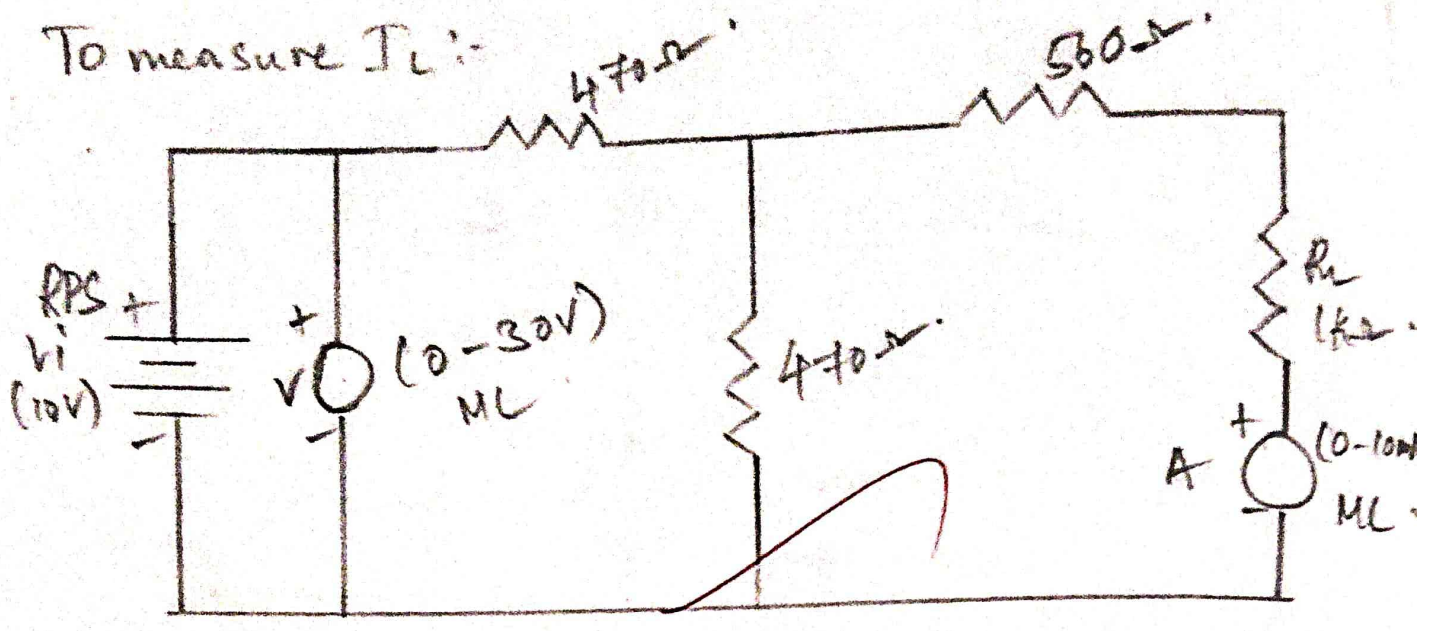


# CIRCUIT DIAGRAM :- VERIFICATION OF THEVENIN'S THEOREM.


To measure  $I_L$  :-

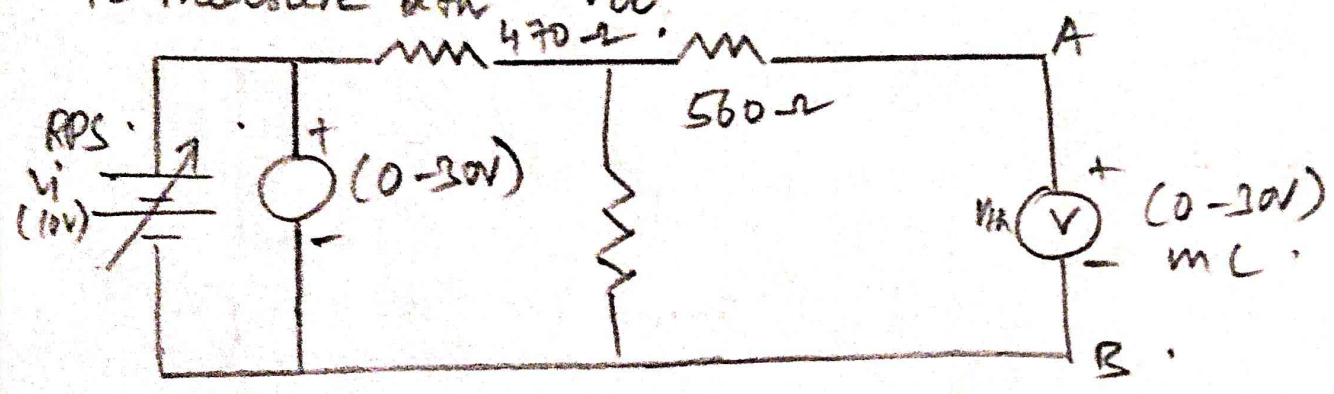

To measure  $R_{th}$  or  $V_{oc}$  :-



to measure  $R_{th}$  or  $R_N$  :-

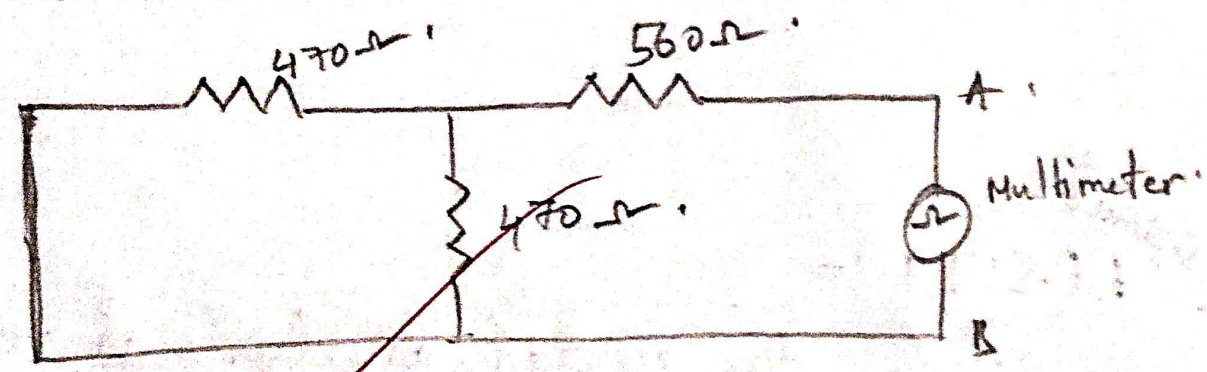

thevenin's equi circuit :-

