

TABULAR COLUMN:-

to measure.

V_p (volts)	V_L (milliamps).
10	2.8.
10	2.8.

TABULAR COLUMN: 2.

to measure R_{th} or R_N .

for circuit diagram 2, $R_{th} = 80\Omega$.

TABULAR COLUMN: 3.

to measure $V_{th} = V_{oc}$.

V_i (volts)	V_{th} (volts).
10	5.14.

MODEL CALCULATIONS:-

Practical value of I_N from tabulation.

$$I = 2.3 \text{ mA}$$

Verification of the venin's theorem.

$$I_N = V_{th} / (R_{th} + R_h) = 2.22 \text{ mA}.$$